

EN3021 Group Project - Progress as of OCT03

210415N Navarathne D.M.G.B.
210594J Senevirathne I.U.B.
210609M Silva M.K.Y.U.N.

October 3, 2024

Current status: 20% Complete

Completed Parts

Following parts of the project have been completed as of October 03:

- The paper design of the single-cycle micro-architecture
- Control signals for each class of instruction
- Planning of hardware implementation of the following components
 - Instruction and data memories
 - Registry file
 - ALU

Paper Design of the Single-cycle Micro-architecture

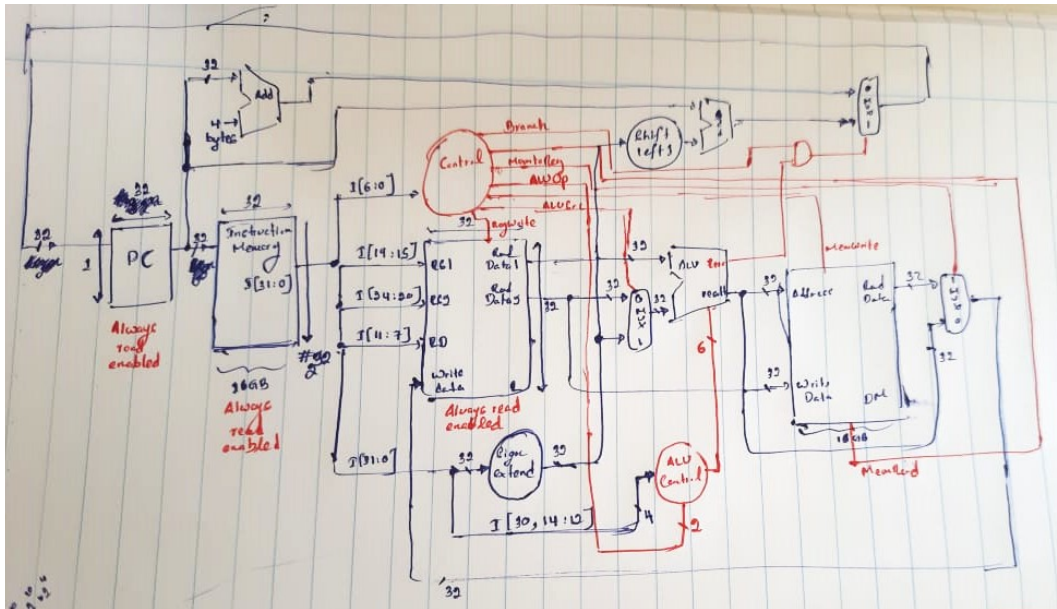


Figure 1: Paper design

Control Signals

Here there's the following set of control signals:

- Branch
- MemRead
- MemtoReg
- ALUOp[1:0]
- MemWrite
- ALUSrc
- RegWrite

And these signals change according to each instruction class as below:

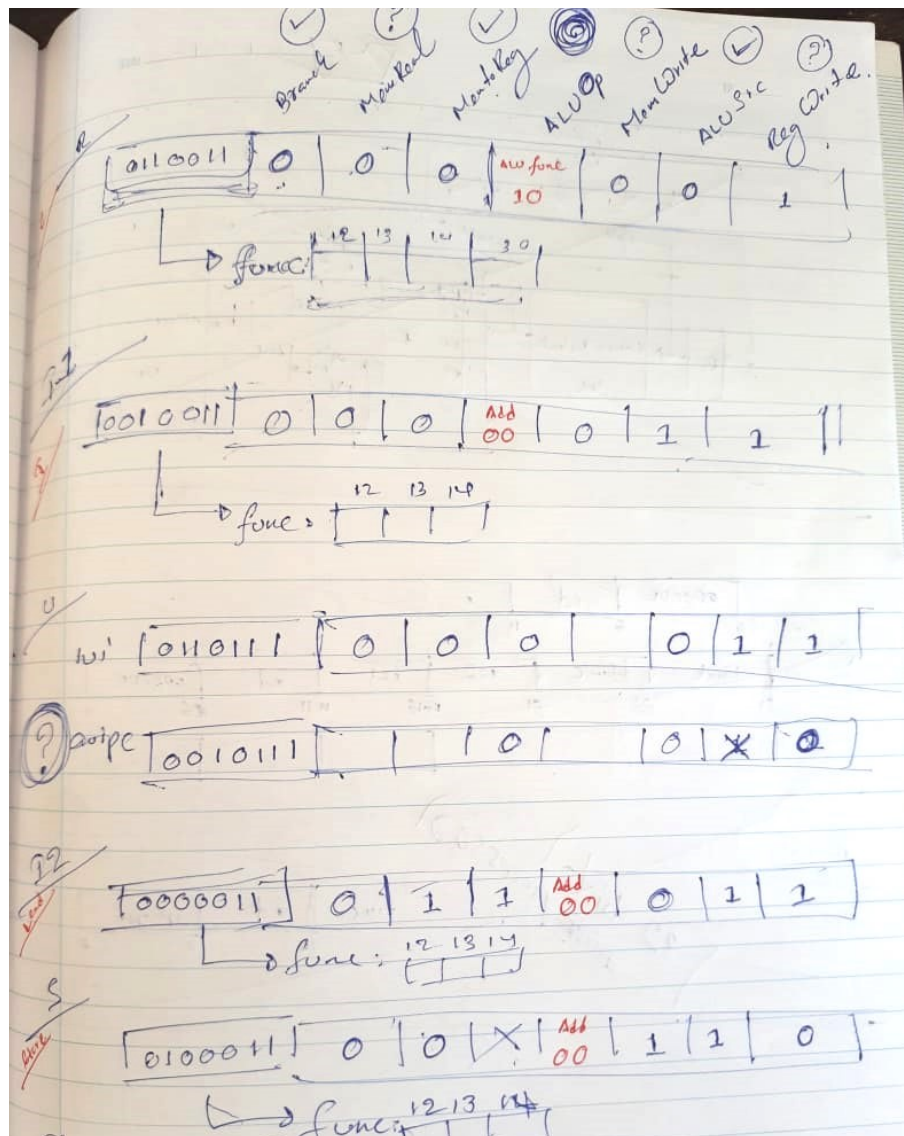


Figure 2: Control signals

 


Figure 3: Control signals

Hardware Implementation

The rough architecture of some components were done as below:

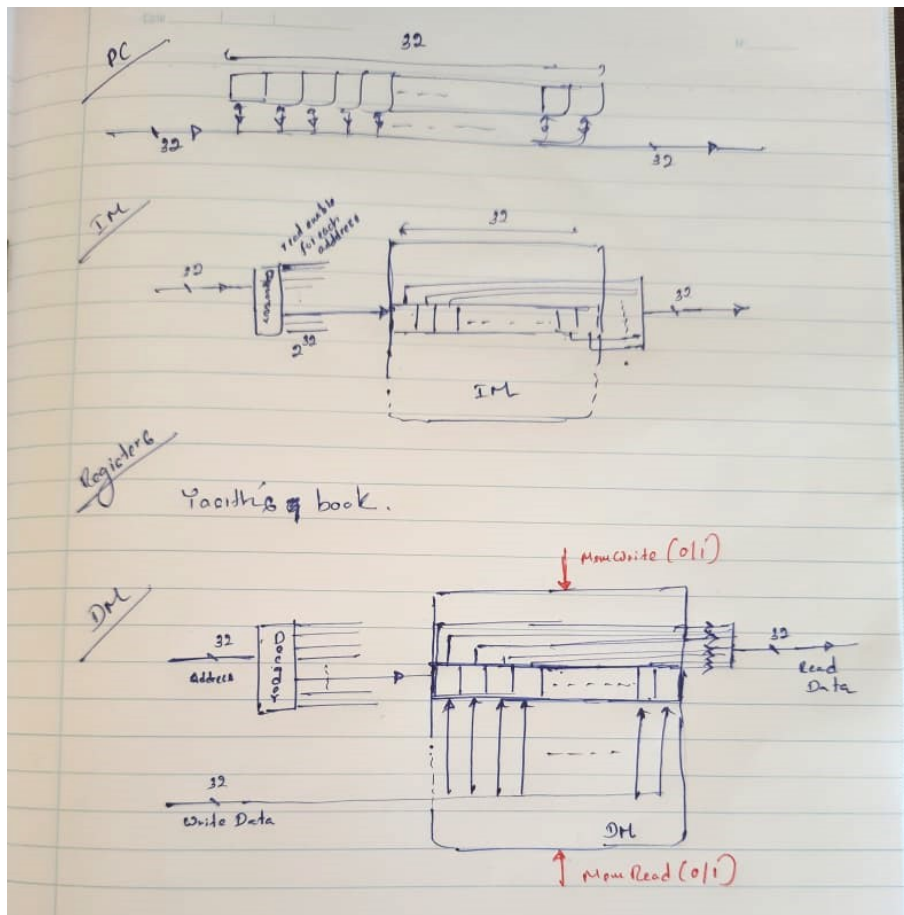


Figure 4: Implementation of PC, IM and DM

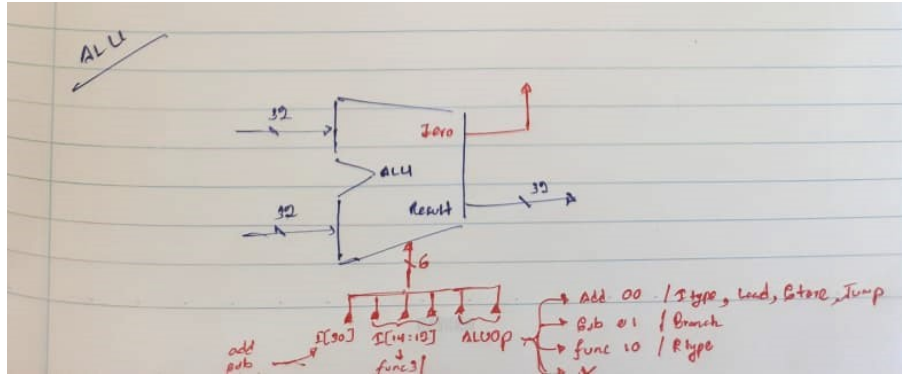


Figure 5: Implementation of the ALU

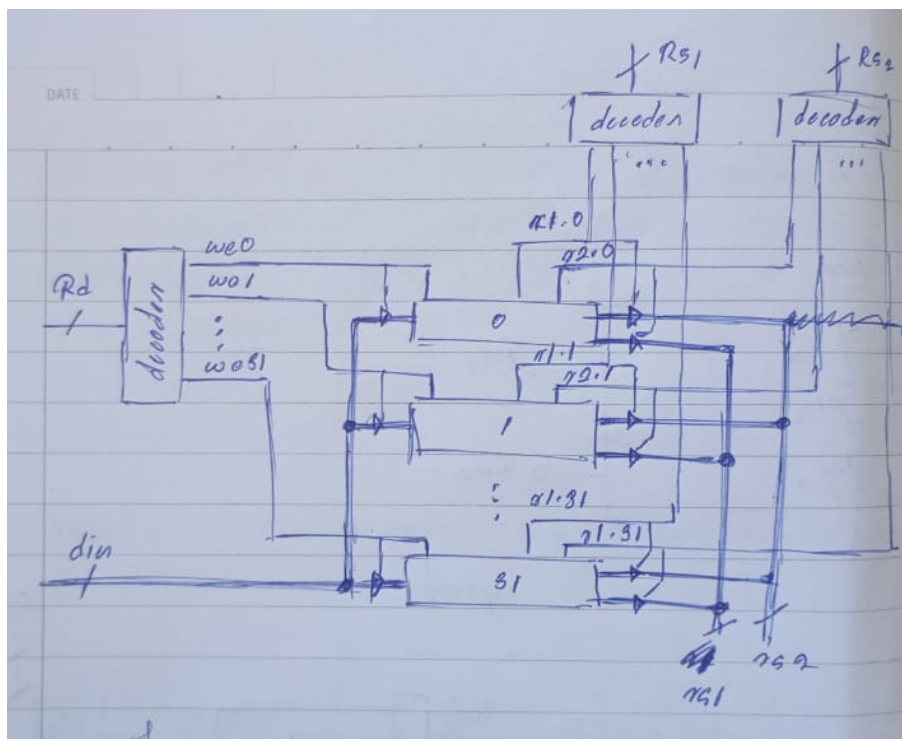


Figure 6: Implementation of the Registry File

Members' Contribution

The paper design part was done together by all team members.